

IV SEMESTER - ELECTRONICS

LAB

- ① Explain inverting operational Amplifier
- ② Explain Non-inverting operational Amplifier
- ③ Explain Differential Amplifier circuit in detail
- ④ Draw the circuit diagram of Summing operational amplifier
- ⑤ Explain Subtractor of Amp
- ⑥ Explain Integrator of Amp
- ⑦ Discuss Comparator of Amp
- ⑧ Explain Second order differential equations of op-Amp
- ⑨ Explain sine wave generator
- ⑩ Square wave generator
- ⑪ Draw the circuit diagram of Astable multivibrator using IC-555
- ⑫ Draw the circuit diagram of Monostable multivibrator using IC-555
- ⑬ What is need for modulation. How many types of modulations are there. Explain different degrees of modulation

(14) write down the equation for Amplitude modulation and draw the frequency spectrum diagram and explain it.

(15) ~~the~~ Draw the circuit diagram of Amplitude modulator and explain the Amplitude modulation in detail. And obtain the mathematical expression for it.

(16) Define Demodulation. Explain diode detector (or) linear diode detector (demodulation) circuit and obtain mathematical expression.

(17) Explain simple frequency modulator circuit.

(18) Explain detector diode FM modulator.

(19) Basic reactance modulator.

(19) Double discriminator demodulator circuit in FM.

(20) Ratio detector.

Short Questions

- ① Ideal characteristics of op-amp
- ② AC voltage follower
- ③ DC voltage follower
- ④ Parameters of op-amp
- ⑤ write a short notes on differentiator circuit
- ⑥ logarithmic op-amp
- ⑦ Draw the pin diagram of IC-555 and explain
- ⑧ High pass filter and low pass filter
- ⑨ Modulation index, modulation factor, percentage modulation - definitions
- ⑩ Need for demodulation
- ⑪ Common mode rejection ratio (CMRR)
- ⑫ Slew rate - notes
- ⑬ write a short notes on carrier swing
- ⑭ Define frequency modulation with neat diagram
- ⑮ Draw frequency spectrum of FM
- ⑯ Define Amplitude modulation with neat diagrams
- ⑰ write a short notes on power in AM.